

Name :

Roll No. :

Invigilator's Signature :

CS/BCA/SEM-1/BCA-101/2013-14

2013

DIGITAL ELECTRONICS

Time Allotted : 3 Hours

Full Marks : 70

The figures in the margin indicate full marks.

*Candidates are required to give their answers in their own words
as far as practicable.*

GROUP - A

(Multiple Choice Type Questions)

1. Choose the correct alternatives for the following : $10 \times 1 = 10$

i) Excess-3 code representation of decimal 984 is

a) 1011 1010 1101 b) 1100 1011 0111

c) 1110 1001 1010 d) 1101 1111 0111

ii) Hexadecimal equivalent of $(1586)_{10}$ is

a) $(362)_{16}$ b) $(623)_{16}$

c) $(632)_{16}$ d) $(263)_{16}$

iii) 2's compliment of 1010111 is

a) 0101001 b) 0110110

c) 0101100 d) 0101101

1057

[Turn over

CS/BCA/SEM-1/BCA-101/2013-14

- iv) A function of three variables $F(A, B, C) = \Sigma(1, 3, 5, 6)$ is given by
- a) an 8-to-1 multiplexer
 - b) two 4-to-1 multiplexer
 - c) one 4-to-1 multiplexer
 - d) none of these.
- v) Multiplexer is also known as
- a) Data selector
 - b) Data distributor
 - c) Multiplexer
 - d) Encoder.
- vi) Parallel Binary Adders are
- a) combinational logic circuit
 - b) sequential logic circuit
 - c) both (a) and (b)
 - d) none of these.
- vii) A Half Adder adds bits.
- a) 16
 - b) 10
 - c) 8
 - d) 2.
- viii) Control Unit does not process data.
- a) true
 - b) false
 - c) unpredictable
 - d) none of these.
- ix) $(ABC + \overline{A}BC + A\overline{B}C)$ is equal to
- a) $A(B + C)$
 - b) $\overline{A}(B + C)$
 - c) $A(B + \overline{C})$
 - d) $A(\overline{B} + C)$
- x) Race Condition is avoided by
- a) J-K flip-flop
 - b) Master-Slave flip-flop
 - c) D flip-flop
 - d) S-R flip-flop.

CS/BCA/SEM-1/BCA-101/2013-14

GROUP - B

(Short Answer Type Questions)

Answer any *three* of the following. $3 \times 5 = 15$

2. Draw the logic symbol, Boolean expression and truth table of NOR and NAND gates. $1 + 2 + 2$
3. State and prove De Morgan's theorem in Boolean algebra. $2 + 3$
4. Represent the decimal number '27' in
 - a) Binary code
 - b) BCD code
 - c) Octal code
 - d) Hexadecimal code
 - e) Gray code. $1 + 1 + 1 + 1 + 1$
5. Prove the following logical equation using Boolean algebra :
 $(A+BC).(B+AC) = BC + AC$
6. Realize the EX-OR logic operation using either NAND gate or NOR gate.
7. Discuss the function of T-type flip-flop with the help of graphic symbol and characteristic table. $3 + 2$

GROUP - C

(Long Answer Type Questions)

Answer any *three* of the following. $3 \times 15 = 45$

8. a) Write down the truth table and logic symbol of a 3-input OR gate.
- b) Using NOR gates, design Full Adder and describe with diagram.
- c) Explain Universal Gate.
- d) Express the function $Y = A + \overline{BC}$ in a canonical SOP form. $2 + 5 + 5 + 3$

CS/BCA/SEM-1/BCA-101/2013-14

9. a) Using *K*-map method simplify the following Boolean function and obtain minimal SOP expression :
$$Y = \sum_m(0,2,3,6,7) + \sum_d(8,10,11,15).$$
- b) Implement the Boolean function $F(A,B,C,D) = \sum_m(0,1,3,8,9,15)$ using two 4-to-1 multiplexer and one OR gate.
- c) Describe the application of Data Distributor.
- d) What is Decoder ? 6 + 6 + 2 + 1
10. a) Explain the concept of parity checking.
- b) Write down the 4-bit gray code in the ascending order of its decimal value.
- c) Design a synchronous Mod-12 down-counter using J-K flip-flops. 5 + 5 + 5
11. a) Design and implement Mod-6 synchronous counter considering lock-out problem. Is the counter self-starting ?
- b) Using the logic diagram convert a J-K flip-flop to a *D* flip-flop and *T* flip-flop.
- c) Explain the difference between Ring and Johnson counter with proper state and a circuit diagram. 7 + 5 + 3
12. a) What do you mean by race condition in flip-flop ?
- b) Design a Master-Slave flip-flop and discuss its operation.
- c) Design and explain 4 bit Parallel Adder/Subtractor. 3 + 5 + 7