



MAULANA ABUL KALAM AZAD UNIVERSITY OF TECHNOLOGY, WEST BENGAL

Paper Code : BCA-101

DIGITAL ELECTRONICS

Time Allotted : 3 Hours

Full Marks : 70

The figures in the margin indicate full marks.

Candidates are required to give their answers in their own words as far as practicable.

GROUP - A

(Multiple Choice Type Questions)

1. Choose the correct alternatives for the following :

10 × 1 = 10

i) The Boolean equation of AND operation is

a) $Y = \bar{A}$

b) $Y = AB$

c) $Y = A + B$

d) None of these.

ii) The logical expression $Y = A + AB$ is equivalent to

a) $Y = A$

b) $Y = AB$

c) $Y = \bar{AB}$

d) $Y = A + B.$

iii) The BCD equivalent of 57 is

a) 111001

b) 01010111

c) ^{64 21} 101111

d) 10001010.

- x) The race around condition will be avoided by
- J-K flip-flop
 - S-R flip-flop
 - Master-Slave flip-flop
 - None of these.

GROUP - B

(Short Answer Type Questions)

Answer any *three* of the following. $3 \times 5 = 15$

- Draw a full adder circuit as combination of 2 half adders.
- State De Morgan's law and prove it for 2 variables.
- Evaluate $(7352)_{10} - (9456)_{10}$ using 9's complement.
 - State Duality principle.
- Minimize the following Boolean expression using K-map.

$$F(A, B, C, D) = \sum(0, 1, 3, 6, 8, 10, 11, 13, 15).$$
- Design a 4-bit parallel-in parallel-out (PIPO) shift register.

GROUP - C

(Long Answer Type Questions)

Answer any *three* of the following. $3 \times 15 = 45$

- Represent the decimal number 45 in
 - Hexadecimal code
 - Gray code
 - BCD code.
 - Which gates are called universal gates and why?
 - Design a 2×4 decoder. Give truth table and draw circuit diagram using basic gates.

d) Implement the expression using a Multiplexer.

$$F(A, B, C, D) = \sum(0, 1, 4, 5, 7, 9, 11, 13, 15).$$

$$3 + 5 + 4 + 3$$

8. a) What is combinational circuit ?

b) Differentiate between combinational and sequential circuits.

c) Explain the functionality of clocked JK flip-flop. Give truth table and diagram.

d) Convert SR to JK flip-flop. $2 + 3 + 5 + 5$

9. a) What is register ?

b) Design an decimal to binary encoder.

c) What do you mean by Johnson counter ?

10. What do you mean by race around condition in flip-flop ? Design a J-K flip-flop and discuss its operation. Design and explain the functioning of BCD adder circuit. $5 + 5 + 5$

11. Write short notes on any *three* of the following : 3×5

a) Universal Gate

b) Multiplexer

c) PAL and PLA

d) Excitation Table

e) Full adder using Half-adder.

