



MAULANA ABUL KALAM AZAD UNIVERSITY OF TECHNOLOGY, WEST BENGAL

Paper Code : BCAC 102 Digital Electronics

UPID : 100048

Full Marks :70

Time Allotted : 3 Hours

The Figures in the margin indicate full marks.

Candidate are required to give their answers in their own words as far as practicable

Group-A (Very Short Answer Type Question)

[1 x 10 = 10]

1. Answer any ten of the following :

- (i) $x * (y + z) = (x * y) + (x * z)$. (this equation represents which boolean property)
- (ii) _____ is formed by multiplying(AND operation) the sum terms
- (iii) simplify : $Y=A'B' + A'B+AB$ (using K map)
- (iv) Draw the block diagram of half adder
- (v) convert $(30)_{10}$ to its equivalent BCD
- (vi) The other name of bistable-multivibrators is
- (vii) $y = A.B$ The dot identifies
- (viii) proof that $yx + x = x$
- (ix) SOP is formed by considering all the minterms, whose output is _____
- (x) According to DE Morgan's law, Inverting the inputs of the AND gate convert it into _____ gate
- (xi) Assume number is using 32-bit format which reserve 1 bit for the sign, 15 bits for the integer part and 16 bits for the fractional part.
Then, -43.625 is represented in fixed point representation as
- (xii) $Y = (A.B)'$ represents which gate

Group-B (Short Answer Type Question)

Answer any three of the following

[5 x 3 = 15]

2. What is Floating-Point Representation ? Give example [5]
3. Write the three basic gates [5]
4. Discuss the two universal gates [5]
5. Define de morgan's law ? with example [5]
6. Define duality principle with example [5]

Group-C (Long Answer Type Question)

Answer any three of the following

[15 x 3 = 45]

7. (a) Define the two universal gate with proper symbol and truth table [8]
(b) Write the two special gate with proper symbol and truth table [7]
8. (a) Explain the following Axioms [8]
a) Closure Property
b) Identity element
c) Commutative property
d) Cardinality Bound.
(b) Discuss the following axioms and show that it is true [7]
a) Distributive Property
b) Complement Element
9. (a) Write any two non weighted code in details [8]
(b) Discuss BCD code and any two alphanumeric codes [7]
10. (a) Implement OR , AND, NOT and NOR using NAND gate [8]
(b) Implement EX-NOR and NAND using NOR gate [7]

11. Simplify the following expression using K-map method

a) $y = m_1 + m_5 + m_{10} + m_{11} + m_{12} + m_{13} + m_{15}$

b) $y = ABCD + AB'C'D' + AB'C + AB$

<https://www.makaut.com>

Whatsapp @ 9300930012

Send your old paper & get 10/-

अपने पुराने पेपर्स भेजे और 10 रुपये पायें,

Paytm or Google Pay से

<https://www.makaut.com>