



**ENGINEERING & MANAGEMENT EXAMINATIONS, DECEMBER - 2008**  
**DIGITAL ELECTRONICS**  
**SEMESTER - 1**

Time : 3 Hours ]

[ Full Marks : 70

**GROUP - A****( Multiple Choice Type Questions )**

1. Choose the correct alternatives for any ten of the following :  $10 \times 1 = 10$
- $(1100 \cdot 1011)_2 = (?)_{10}$ 
    - 10.6785
    - 11.6578
    - 12.6875
    - 13.6785.
  - 2's complement of 10101100 is
    - 11001010
    - 01010011
    - 01010100
    - 01011001.
  - $(247 \cdot 36)_8 = (?)_{16}$ 
    - A7.78
    - 1A7.36
    - B7.87
    - 1B7.36.
  - MBR, in reference to memory management is
    - Memory Broad Register
    - Memory Buffer Relay
    - Memory Buffer Register
    - None of these.
  - Output of NAND gate is 1, if and only if
    - all inputs are 1
    - any input is 1
    - all inputs are 0
    - any input is 0.



vi)  $A + \bar{A} = ?$

- |      |                |
|------|----------------|
| a) 1 | b) 0           |
| c) A | d) $\bar{A}$ . |

vii) If the no. of states of a counter is 8, then the no. of flip-flops is

- |      |       |
|------|-------|
| a) 8 | b) 3  |
| c) 4 | d) 6. |

viii)  $(A.B + \bar{A}.B + \bar{A}.\bar{B})$  is equal to

- |                  |                  |
|------------------|------------------|
| a) $A + \bar{B}$ | b) $\bar{A} + B$ |
| c) $A + B$       | d) 1.            |

ix) Karnaugh Map is used to

- a) simplify Boolean function
- b) design Boolean function
- c) evaluate Boolean function
- d) none of these.

x) A multiplexer has

- |                 |                    |
|-----------------|--------------------|
| a) single input | b) multiple output |
| c) no output    | d) single output.  |

xi) Output of R-S ( NAND ) flip-flop, for R = 1 & S = 1 is

- a) set
- b) reset
- c) race
- d) no change.

xii) Subtracting 1111 from 11000 will result to

- |         |          |
|---------|----------|
| a) 1000 | b) 1100  |
| c) 1001 | d) 1011. |

**GROUP - B****( Short Answer Type Questions )**

Answer any three of the following.

 $3 \times 5 = 15$ 

2. Apply K-map to obtain the minimal form for the function :

$$F(A, B, C, D) = \Sigma(0, 4, 5, 7, 8, 9, 13, 15)$$

$$d(A, B, C, D) = \Sigma(1, 2, 6, 10)$$

3. Draw a half-adder circuit and describe its operations.

4. Design a 4-bit up-down counter.

5. Prove the following logical equation using Boolean algebra :

$$(A+BC) \cdot (B+A\bar{C}) = BC + A\bar{C}$$

6. i) Subtract  $(7489)_{10} - (2485)_{10}$  using 10's complement method.

- ii) What is a Multiplexer ? Why is it called "Data selector" ?

**GROUP - C****( Long Answer Type Questions )**

Answer any three of the following questions.

 $3 \times 15 = 45$ 

7. a) Represent the decimal number "27" in

- i) BCD code

- ii) Octal code

- iii) Gray code.

- b) Draw the block diagram of a digital multiplexer and explain its function.

- c) Give the functional truth table of a 4 : 1 multiplexer and realize it using basic gates AND, OR and NOT.

- d) Implement the expression using a multiplexer :

$$f(A, B, C, D) = \Sigma m(0, 2, 3, 6, 8, 9, 12, 14)$$

 $3 + 4 + 4 + 4$ **11006 (3/12)**



8. a) What do you mean by a sequential circuit ?  
 b) What are synchronous & asynchronous sequential circuits ?  
 c) Explain the functionality of D-flip-flop. Give the truth table, State diagram.  
 d) What do you mean by Edge-triggering & Level-triggering in flip-flops ?

2 + 3 + 5 + 5

9. a) What is a flip-flop ?  
 b) What are the uses of flip-flops ?  
 c) Give the circuit diagram of a J-K flip-flop.  
 d) Give the truth tables of S-R & J-K flip-flops.

2 + 3 + 4 + 6

10. a) Given the following truth table :

| Inputs |   |   | Outputs |    |
|--------|---|---|---------|----|
| x      | y | z | F1      | F2 |
| 0      | 0 | 0 | 0       | 0  |
| 0      | 0 | 1 | 1       | 0  |
| 0      | 1 | 0 | 1       | 0  |
| 0      | 1 | 1 | 0       | 1  |
| 1      | 0 | 0 | 1       | 0  |
| 1      | 0 | 1 | 0       | 1  |
| 1      | 1 | 0 | 0       | 1  |
| 1      | 1 | 1 | 1       | 1  |

- i) Obtain the simplified functions in sum of products.  
 ii) Obtain the simplified functions in product of sums.

- b) Design a BCD to Excess-3 Code converter.

8 + 7

11. a) Explain different types of RAM and ROM.

- b) Write short notes on any two of the following :

- i) Parity checker  
 ii) Ring counter  
 iii) Magnitude comparator.

7 + ( 2 × 4 )

END