

Name : .....

Roll No. : .....

Invigilator's Signature : .....

**CS/BCA/SEM-1/BCA-101/2010-11**

**2010-11**

## **DIGITAL ELECTRONICS**

**Time Allotted : 3 Hours**

**Full Marks : 70**

*The figures in the margin indicate full marks.*

*Candidates are required to give their answers in their own words  
as far as practicable.*

### **GROUP - A**

#### **( Multiple Choice Type Questions )**

1. Choose the correct alternatives for any ten of the following :  $10 \times 1 = 10$

- i) In which of the following base systems is 789 not a valid number ?
- a) Base 5
  - b) Base 16
  - c) Base 8
  - d) Base 3.
- ii) Storage of 1 kB means the what number of bytes ?
- a) 1000
  - b) 964
  - c) 1024
  - d) 1064.

iii) Pick out the correct statement :

- a) In a positional number system, each symbol represents the same value irrespective of its position
- b) The highest symbol in a position number system is a value equal to the number of symbols in the system
- c) It is not always possible to find the exact binary
- d) Each hexadecimal digit can be represented as a sequence of three binary symbols.

iv) The binary code of  $(21.125)_{10}$  is

- a) 10101.001
- b) 10100.001
- c) 10101.010
- d) 10100.111

v) Race condition is avoided by

- a) J-K flip-flop
- b) S-R flip-flop
- c) master-slave flip-flop
- d) none of these.

vi) Which one is sequential circuit ?

- a) multiplexer
- b) decoder
- c) priority encoder
- d) counter.

vii) Which is correct ?

- a)  $A + \overline{A}B = A + B$
- b)  $A + 1 = A$
- c)  $A + \overline{A} = A$
- d)  $\overline{A}/A = A$

viii) Decimal digits can be converted to binary code using

- a) Decoder
- b) Encoder
- c) Mux
- d) DeMux.

- ix) Carry of a full adder is a
- dual function
  - self dual function
  - non-symmetric function
  - none of these.
- x) Every flip-flop is defined by
- characteristic equation
  - excitation table
  - both of these
  - none of these.
- xi) Immediate Access Storage Device is the name of
- primary memory
  - secondary memory
  - hard disk
  - pen drive.
- xii) Control unit does not process data.
- False
  - True
  - Unpredictable
  - None of these.
- xiii) If there are three inputs then the number of input combinations will be
- four
  - eight
  - six
  - two.
- xiv) Excess-3 Code representation of decimal 59 is
- 01100110
  - 10001100
  - 01011001
  - 11000110.
- xv) Hexadecimal equivalent of  $(26.25)_{10}$  is
- A6.4
  - 1A.4
  - FA.4
  - 1A.25

**GROUP - B**

**( Short Answer Type Questions )**

Answer any three of the following.  $3 \times 5 = 15$

2. Implement XOR operation using four 2-input NAND gates.  
Verify the output for different combinations of inputs.
3. Write down the BCD code of  $(9612)_{10}$ . Add two numbers  $(6952)_{10}$  and  $(1589)_{10}$  using BCD codes and obtain the result also in BCD.
4. a) Find out the dual and the complement of the following Boolean function :

$$F = ABC + \bar{A} \bar{B} C + \bar{A} B \bar{C} + A \bar{B} \bar{C}$$

- b) Simplify the following Boolean expression

$$(X + Y)(\bar{X} + Y + Z)(\bar{X} + Y + \bar{Z})$$

to minimum number of literals using algebraic method.

5. a) Prove that the multiplexer is a universal logic module.
- b) Use 4-to-1 MUX and other necessary logic gate to design a full-subtractor.
6. a) What is the advantage of JK flip-flop over SR flip-flop ?  
b) Write the Maxterm form of the following function :

$$F = XY + \bar{X}Z$$


**GROUP - C**

**( Long Answer Type Questions )**


Answer any *three* of the following.  $3 \times 15 = 45$

7. a) Draw the truth table for a three input adder. Explain clearly the meaning of the input and the output symbols in the truth table. Write the Boolean expressions for the sum and carry. 5
- b) Use a Karnaugh map to find the minimum sum of products for the expression  $X = A'B'C + AB'C + A'BC + ABC'$  5
- c) Simplify the following expressions using Boolean algebra : 5
- $AB + A(B+C) + B(B+C)$
  - $A'BC + B'CD + AC + A'B'CD'$
8. a) State the main differences between sequential and combinational circuits. 2
- b) Draw the truth table and logic circuit of a Full Subtractor. Using Karnaugh map find out the expression for difference ( $D$ ) and borrow ( $B$ ). 4 + 3
- c) Implement the Boolean function  $F = (A, B, C, D) = \sum(0, 1, 3, 4, 8, 9, 15)$  using  $8 \times 1$  multiplexer with  $A, B$  and  $D$  connected to select lines  $s_2, s_1, s_0$  respectively. 6

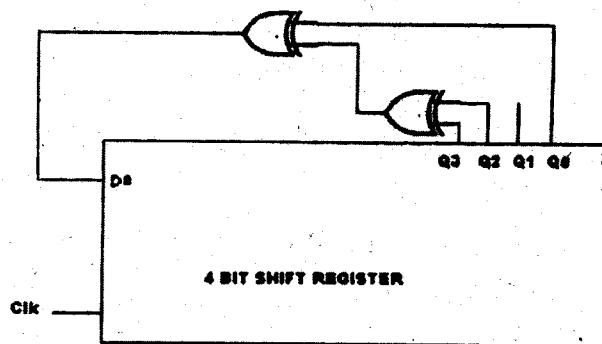9. a) Define flip-flop and its propagation delay. 4
- b) Using the logic diagram convert a J-K flip-flop to a D flip-flop and T flip-flop. 5
- c) Design a J-K master-slave flip-flop with circuit diagram and give the truth table. 6
10. a) What is the usefulness of excitation table of the flip-flop ? 3
- b) The 4-bit shift register is initialised to 001. After how many clock pulses is the register re-initialised to same value ? 6



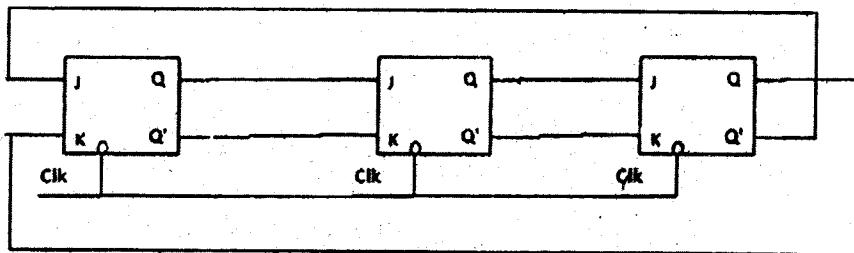- c) Determine the modulus of the following counter. 6



11. Write short notes on any *three* of the following :  $3 \times 5$

- a) Decoder
  - b) Shift register
  - c) PROM
  - d) Priority Checker
  - e) Ring counter.
-