

2011

DIGITAL ELECTRONICS

Time Allotted : 3 Hours

Full Marks : 70

The figures in the margin indicate full marks.

Candidates are required to give their answers in their own words as far as practicable.

GROUP - A

(Multiple Choice Type Questions)

1. Choose the correct alternatives for any *ten* of the following :

10 × 1 = 10

- i) $(A + A' B + B')$ is equal to
- | | |
|------|---------|
| a) A | b) B' |
| c) 1 | d) 0. |
- ii) (10110) is equivalent to
- | | |
|-------|--------|
| a) 20 | b) 22 |
| c) 24 | d) 18. |
- iii) A BCD counter is an example of
- | |
|---------------------------|
| a) a decade counter |
| b) a full modules counter |
| c) both (a) and (b) |
| d) none of these. |

- xi) Full adder can add
- a) two binary numbers b) three binary numbers
c) four binary numbers d) none of these.
- xii) MOD - 10 counter can count up to
- a) 9 b) 10
c) 8 d) none of these.

GROUP - B**(Short Answer Type Questions)**

Answer any *three* of the following. $3 \times 5 = 15$

2. State and prove De-Morgan's theorems.
3. Express the Boolean function $F = AB + \bar{A}C$ in a product of maxterm form.
4. Define multiplexer. Why is it called "Data Selector" ? $3 + 2$
5. Use 4 : 1 MUX and other necessary logic gates to design a full adder.
6. What is flip-flop ? What is meant by race condition ? $1 + 4$

GROUP - C**(Long Answer Type Questions)**

Answer any *three* of the following. $3 \times 15 = 45$

7. a) Using K-map method, simplify the following Boolean function and obtain minimal SOP expression :
 $Y = \sum m (0, 2, 3, 6, 7) + \sum d (8, 10, 11, 15)$.
- b) Implement the Boolean Function $F = (A, B, C, D) = \sum m (0, 1, 3, 8, 9, 15)$ using two 4 - to-1 multiplexer and one OR gate.
- c) Design a gray code to binary converter circuit of 5 bits.
What is nibble ? $5 + 5 + (4 + 1)$

8. a) Design a half adder circuit using minimum number of 2-input NOR gates only. Write Down the truth table and Boolean functions also.
- b) Convert a D flip-flop to a J-K flip-flop. You can use additional circuiting if required.
- c) What is full subtractor ? Explain its basic structure with proper logic diagrams and truth tables. $5 + 5 + 5$
9. a) Convert the following :
- i) $(AC15)_{16} = (?)_{10}$
- ii) $(1011001)_2 = (?)_{10}$
- b) Discuss about the design of an odd parity generator.
- c) Explain the concept of parity checking.
- d) What is the advantage of J-K flip-flop over SR flip-flop. $5 + 5 + 2 + 3$
10. a) What is the difference between sequential and combinational circuit ?
- b) Describe the propagation delay of a flip-flop.
- c) Express the Boolean function $F = AB + A' C$ in a product of maxterm form. $5 + 5 + 5$
11. a) Draw a block diagram and write truth table of a D flip-flop.
- b) Compare asynchronous and synchronous counter.
- c) Use 4 to 1 MUX and other necessary logic gate to design a full adder. $5 + 5 + 5$
12. Write short notes on any *three* of the following : 3×5
- a) EPROM
- b) D flip-flop
- c) Ripple counter
- d) Encoder
- e) 4-bit parallel Adder.