



Name : .....

Roll No. : .....

Invigilator's Signature : .....

**CS/BCA/SEM-1/BCA-101/2012-13**

**2012**

**DIGITAL ELECTRONICS**

Time Allotted : 3 Hours

Full Marks : 70

*The figures in the margin indicate full marks.*

*Candidates are required to give their answers in their own words as far as practicable.*

**GROUP - A**

**( Multiple Choice Type Questions )**

1. Choose the correct alternatives of the following :

10 × 1 = 10

- i) The Boolean equation of AND operation is
  - a)  $Y = \bar{A}$
  - b)  $Y = AB$
  - c)  $Y = A + B$
  - d) None of these.
- ii) The logical expression  $Y = A + \bar{A}B$  is equivalent to
  - a)  $Y = AB$
  - b)  $Y = \bar{A}B$
  - c)  $Y = A + \bar{B}$
  - d)  $Y = A + B$ .
- iii) The BCD equivalent of 57 is
  - a) 111001
  - b) 01010111
  - c) 101111
  - d) 10001010.
- iv) In the BCD code, the decimal number 123 is written as
  - a) 11011
  - b) C3
  - c) 001010011
  - d) 000100100011.



- v) A carry look-ahead adder is frequently used for addition, because it
- a) is faster
  - b) is more accurate
  - c) uses fewer gates
  - d) costs less.
- vi) A combinational circuit is one in which the output depends on the
- a) input combination at a time
  - b) previous output and input combination
  - c) previous input and input combination at a time
  - d) present output and previous output.
- vii) Each individual term in standard SOP form is called as
- a) Maxterm
  - b) Minterm
  - c) Midterm
  - d) None of these.
- viii) A decoder with 64 output lines has \_\_\_\_\_ data inputs.
- a) 64
  - b) 1
  - c) 6
  - d) None of these.
- ix) The number of flip-flops required to build a Mod-15 counter is
- a) 4
  - b) 5
  - c) 6
  - d) 7.
- x) The full form of CCD is
- a) Charged-couple disk
  - b) Charge-coupled device
  - c) Cache coupled device
  - d) None of these.



**GROUP – B**

**( Short Answer Type Questions )**

Answer any *three* of the following.  $3 \times 5 = 15$

2. Draw a full adder circuit as combination of 2 half adders.
3. State Demorgan's law and prove it for 2 variables.
4. a) Evaluate  $(7352)_{10} - (9456)_{10}$  using 9's compliment.  
b) State Duality principle.
5. Minimize the following Boolean expression using K-map.  
 $F(A,B,C,D) = \Sigma(0,1,3,6,8,10,11,13,15)$
6. Design a 4 bit parallel-in parallel-out (PIPO) shift register.

**GROUP – C**

**( Long Answer Type Questions )**

Answer any *three* of the following.  $3 \times 15 = 45$

7. a) Represent the decimal number 45 in
  - i) Hexadecimal code
  - ii) Gray code
  - iii) BCD code.
- b) Which gates are called universal gates and why ?
- c) Design a  $2 \times 4$  decoder. Give truth table and draw circuit diagram using basic gates.
- d) Implement the expression using a Multiplexer.

$$F(A,B,C,D) = \Sigma (0,1,4,5,7,9,11,13,15) \quad 3 + 5 + 4 + 3$$



8. a) What is combinational circuit ?  
 b) Differentiate between combinational and sequential circuit.  
 c) Explain the functionality of clocked JK flip-flop. Give truth table and diagram.  
 d) Convert SR to JK flip-flop. 2 + 3 + 5 + 5
9. a) What is register ?  
 b) Design a decimal to binary encoder.  
 c) What do you mean by Johnson counter ? 3 + 6 + 6
10. a) Given the following truth table.

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

Obtain the SOP and POS form and draw the circuit diagram.

- b) Express the following Boolean expressions :
- i)  $f = AB + A'C$  in POS form.  
 ii)  $f = (A + BC)(B + C' A)$  in SOP form. 8 + 7
11. a) What is the difference between synchronous and asynchronous counter ?  
 b) Write short notes on the following :  
 i) EPROM  
 ii) DRAM.  
 c) What is the difference between SRAM and DRAM ? 4 + 6 + 5

