

MCA-101

COMPUTER ORGANIZATION AND ARCHITECTURE

Time Allotted: 3 Hours

Full Marks: 70

The questions are of equal value.

The figures in the margin indicate full marks.

Candidates are required to give their answers in their own words as far as practicable.

GROUP A

(Multiple Choice Type Questions)

1. Answer all questions. 10×1 = 10
- (i) A full subtractor can be designed with a full adder by
- (A) only changing the circuit
 - (B) adding a NOT with the SUM input
 - (C) adding a NOT with CARRY input
 - (D) none of these
- (ii) How many bits are needed to represent a digit in hexadecimal notation?
- (A) 8
 - (B) 16
 - (C) 4
 - (D) 2
- (iii) Conversion of $(FAFAFA)_{16}$ into octal form is
- (A) 76575372
 - (B) 76575370
 - (C) 7675374
 - (D) 72727272
- (iv) 1-nibble is equal to
- (A) 2 bits
 - (B) 8 bits
 - (C) 4 bits
 - (D) 16 bits

- (v) Which of the following addressing mode is used in 'PUSH B'?
- (A) direct (B) immediate
(C) register (D) register-immediate
- (vi) Which of the following input combinations is not allowed in SR Flip-Flop?
- (A) S = 0, R = 0 (B) S = 1, R = 1
(C) S = 0, R = 1 (D) S = 1, R = 0
- (vii) Gray code for binary 1011
- (A) 1101 (B) 1110
(C) 1001 (D) 0111
- (viii) How many address bits are required for a 1024×8 memory unit?
- (A) 2 (B) 8
(C) 10 (D) 12
- (ix) The basic principle of a Von-Neumann Computer is
- (A) storing both data and program in same memory
(B) storing both data and program in separate memory
(C) storing only data
(D) storing only program
- (x) Which of the following operation is not directly possible in 8085 microprocessor?
- (A) MUL (B) DIV
(C) CMA (D) both (A) and (B)

GROUP B
(Short Answer Type Questions)

Answer any *three* questions.

3×5 = 15

2. With truth table and Boolean function, design a half adder circuit with minimum number of 2-input NOR gates only. 5
3. Differentiate between hardware control and microprogrammed control unit. 5
4. Convert a JK Flip-flop into a D Flip-Flop. You can use additional circuitry, if required. 5
5. (a) Add the following numbers using 2's complement method. +30 and -22 4+1
(b) What is the 2's complement of $(1000\ 1111\ 0001\ 1110)_2$?
6. Explain Associative memory. 5

GROUP C
(Long Answer Type Questions)

Answer any *three* questions.

3×15 = 45

7. (a) Construct a full Subtractor with half adders and an additional gate. 6
(b) Construct XOR using NAND. 3
(c) What is truth table? Why it called so? 3
(d) Design the circuit $AB+BC(B+C)$. 3
8. (a) Write down the De Morgan's Theorem? 3
(b) Simplify using Boolean algebra 6
(i) $(A + (BC)')'$
(ii) $A'BC + AB'C + ABC' + ABC$

- (c) Simplify using K map 6
(i) $(A + AB)$
(ii) $A'B'C + A'BC + AB'C + ABC$
- 9.(a) What is bus speed? 2
(b) What is PLA? 2
(c) Describe basic architecture of a digital computer. 6
(d) Design the circuit using multiplexer $F(A,B,C)=\sum(0,1,3,4,8,9,15)$. 5
- 10.(a) What is micro controller? 3
(b) Write a 8085 instruction code for swap two value. 6
(c) Write a 8085 instruction code for add three number with 200. 6
11. Write short notes on any *three* of the following: 3×5
(a) D flip flop
(b) RAM and ROM
(c) ALU
(d) binary comparator
(e) decoder and encoder
(f) circuit design with multiplexer