

3e

CS/MCA/Sem-1/MCA-101/2004

2004

**COMPUTER ORGANISATION AND ARCHITECTURE**

Time Allotted: 3 hours

Full Marks: 70

The questions are of equal value.

The figures in the margin indicate full marks.

Candidates are required to give their answers in their own words as far as practicable.

**Answer Question No.1 and any six from the rest**

Answer any ten from the following:

1x10

- i) Prove that,  $(a + b'c')'(ab' + abc) = 0$  in Boolean algebra.
- ii) Why is a gated D latch called 'transparent' latch?
- iii) Why demultiplexer is called data distributor?
- iv) If  $A \oplus B = C$ , then show that,  $A \oplus C = B$ .
- v) What is 'miss penalty'?
- vi) "Synchronous counters can be used at higher frequency compared to an asynchronous counters having same MOD-number". Critically comment on the above statement.
- vii) The Program Counter (PC) is called "memory pointer" – Justify your answer.
- viii) What is universal shift register?
- ix) What is the function of ALE in 8085 microprocessor?
- x) The Q and Q' output of an edge triggered JK flip-flop are connected to its J and K inputs and clock is applied. Do you find any similarity with any well known flip-flop?
- xi) "DMA is increasing the performance of CPU." – Justify .
- xii) Can an input port and an output port have the same port address?
- xiii) Express 9407 in BCD.
- xiv) Express  $(7652)_{10}$  in Excess-3 code.

- 2 a) Draw a NAND logic diagram that implements the following function 5  
 $F(A, B, C, D) = \sum (0, 1, 2, 3, 4, 8, 9, 12)$ .
- b) Write down the differences between static RAM and dynamic RAM. 2
- c) Explain the importance of accumulator in microprocessor. 3
- 3 a) Design a half adder circuit using minimum number of 2-input NOR gates only. Write down the truth table and Boolean functions also. 6
- b) Determine the value of x, if  $(211)_x = (152)_8$  2

- c) Subtract using 2's complement : 11001 – 1010 . 2
4. a) Show how a full adder can be converted to a full subtractor with the addition of just one inverter with the full adder circuit. 5  
 b) Design a decimal to BCD encoder. 5
5. a) Convert a D flip-flop to a JK flip-flop. You can use additional circuiting if required. 5  
 b) Design a 64K x 8 memory module using 16K x 1 memory chips. Draw the block diagram only. 5
6. a) Design a synchronous counter with JK flip-flop, which counts the following sequences: 7  
 0, 1, 2, 4, 5, 6 and again back to 0.  
 b) What is the difference between memory mapped I/O and IO-mapped I/O? 3
7. a) Explain Booth's multiplication algorithm with a suitable example. 8  
 b) What is the difference between hardware interrupt and software interrupt? 2
8. a) Design a BCD ripple counter and explain its operation with timing diagram. 7  
 b) How the same buses are worked together as low order address bus and data bus in 8085 microprocessor? 3
9. a) How DMA is initiated and how DMA controller works? 7  
 b) What is instruction cycle? What are the different phases of instruction cycle? 3
10. a) Evaluate the following arithmetic expression using single accumulator organisation instruction and stack organization instruction. 6  

$$X = A - B + C * (D/E)$$
  
 b) How the effective address is calculated in direct address mode and an indirect address mode? 4
11. Write short notes on any two of the following: 5x2  
 (a) Interrupt lines of 8085 microprocessor.  
 (b) Vector processing.  
 (c) Von – Neumann architecture.  
 (d) Addressing modes.

\*\*\*