



ENGINEERING & MANAGEMENT EXAMINATIONS, DECEMBER - 2006
COMPUTER ORGANIZATION AND ARCHITECTURE
SEMESTER - 1

Time : 3 Hours]

[Full Marks : 70

The figures in the margin indicate full marks.

Candidates are required to give their answers in their own words as far as practicable.

Answer Question No. 1 and any four from the rest.

1. Answer any five from the following : 5 × 2 = 10

- i) What are the different flags in 8085 microprocessor ?
- ii) Why is multiplexer called "data selector" ?
- iii) What is cache memory ?
- iv) Add the following numbers using 2's complement method :
+ 49 and - 37.
- v) What is meant by Harvard Architecture ?
- vi) What is the purpose of stack in microprocessor ?
- vii) Define T state, machine cycle and instruction cycle.
- viii) What is hit ratio and miss penalty ?

2. a) $f(A, B, C, D) = \sum m(0, 2, 3, 5, 6, 7, 8, 9) + \sum d(10, 11, 12, 13, 14, 15)$.

Realize the minimised function using only NAND gates. /

- b) A digital computer has a common bus system for K registers, each of n bit capacity. The bus is constructed with multiplexers.
 - i) What size of multiplexers is needed ?
 - ii) How many multiplexers are there in the bus ?
- c) Draw a comparison between RISC and CISC machines. 5 + 5 + 5 = 15



3. a) Give the block diagram of 8085 microprocessor clearly mentioning different functional units.
- b) Draw the timing diagram of the OP CODE fetch machine cycle.
- c) Explain the function of the ALE signal in 8085 microprocessor.
- d) What is the duration of a T-state in 8085 microprocessor ? $6 + 6 + 2 + 1$
4. a) Show how a full adder can be converted to a full subtractor with the addition of just one inverter with the full adder circuit.
- b) Design a decimal to BCD encoder. $8 + 7$
5. a) Design a BCD ripple counter and explain its operation with timing diagram.
- b) Explain Booth's multiplication algorithm with suitable example. $8 + 7$
6. a) With a suitable diagram explain the concept of microprogramming.
- b) What are the different stages of instruction pipelining ?
- c) Define Speedup, Efficiency and Throughput of a pipeline.
- d) What is pipeline staling ? $7 + 2 + 4 + 2$
7. a) What is the difference between a latch and edge triggered flip-flop ?
- b) Draw the circuit diagram of a master-slave JK flip-flop using all NAND gates and explain the circuit operation.
- c) Convert a D flip-flop to a JK flip-flop using additional gates. $3 + 7 + 5$
8. Write short notes on any *three* of the following : $3 \times 5 = 15$
- a) DMA
- b) Vector Processing
- c) Interrupt lines in 8085 microprocessor
- d) von Neumann architecture
- e) Virtual memory.
-
-