



Name : .....

Roll No. : .....

Invigilator's Signature : .....

**CS/MCA/SEM-1/MCA-101/2010-11**  
**2010-11**  
**COMPUTER ORGANIZATION AND**  
**ARCHITECTURE**

Time Allotted : 3 Hours

Full Marks : 70

*The figures in the margin indicate full marks.*

*Candidates are required to give their answers in their own words  
as far as practicable.*

**GROUP – A**

**( Multiple Choice Type Questions )**

1. Choose the correct alternatives for the following :  $10 \times 1 = 10$ 
  - i) A full subtractor can be designed with a full adder by
    - a) only changing the circuit
    - b) adding a not with sum input
    - c) adding a not with carry input
    - d) none of these.
  - ii)  $( 264 )_8 = ( ? )_{10}$ 

a) 2640	b) 128
c) 108	d) 127.
  - iii) 2's complement of 100000 is

a) 011111	b) 100000
c) 11111	d) 111111.





**GROUP – B**

**( Short Answer Type Questions )**

Answer any *three* of the following. 3 × 5 = 15

2. Verify the de Morgan's theorem by means of truth table.
3. a) Express the Boolean function  $F = AB + A'C$  in a product sum.
- b) Express the Boolean function  $F = x + y'z$  in a sum of product form.
4. a) Add the following numbers using 2's complement method : 3  
 $+ 49$  and  $- 37$ .
- b) Perform the subtraction using 2's complement method. 2  
 $11000 - 1101$ .
5. Convert a JK flip-flop into a D flip-flop. You can use additional circuitry, if required.
6. Obtain a minimal product of sum expression for the function given below :

$$F ( w, x, y, z ) = \prod ( 1, 4, 5, 9, 13, 14 )$$

**GROUP – C**

**( Long Answer Type Questions )**

Answer any *three* of the following. 3 × 15 = 45

7. a) Construct a full subtracter with half adders and an addition gate.
- b) Construct XOR using NAND gates only.
- c) What is truth table ? Why is it called so ?
- d) Design the circuit  $AB + BC ( B + C )$ . 6 + 3 + 3 + 3



8. a) Compare two addressing mode and three addressing mode.
- b) Simplify using boolean algebra :
- i)  $(A+(BC)')'$
- ii)  $A'BC + AB'C + ABC' + ABC$ .
- c) Simplify using K map :
- i)  $A + AB$
- ii)  $A'B'C + A'BC + AB'C + ABC$ . 3 + 6 + ( 3 + 3 )
9. a) What is bus speed ?
- b) What is PLA ?
- c) Describe basic architecture of a digital computer.
- d) Design the circuit using multiplexer :  
 $F(A, B, C) = \sum(0, 1, 3, 4, 8, 9, 15)$  2 + 2 + 6 + 5
10. a) What is microcontroller ?
- b) Write a 8085 instruction code for swap two values.
- c) Describe Von Neuman architecture. 3 + 6 + 6
11. Write short notes on any *three* of the following : 3 × 5
- a) Universal gate
- b) DMA controller
- c) ALU
- d) Binary Comparator
- e) Decoder and Encoder.
-